

---

---

The logo for www.eletricatotal.com features the website name in a bold, orange, italicized sans-serif font. The text is centered within a dark, rectangular background that has a subtle, abstract pattern of light and dark shapes, possibly representing electrical sparks or a circuit board.

## Maximum Transfer Theorem in AC Power

---

by [www.eletricatotal.com](http://www.eletricatotal.com)

---

In Chapter 7 we studied this theorem when we only had resistors in a DC circuit. Now let's study it in AC and when there is presence of reactive elements in the circuit. Let's consider an impedance in series with a source of voltage, such that it is a complex impedance. This form, it will be of the type:

$$Z_i = R_i \pm j X_i \quad (1)$$

The load will also be a complex impedance. We will write as:

$$Z_L = R_L \pm X_L \quad (2)$$

To calculate the power dissipated in the load, we will first calculate the electric current that circulates through the circuit. See the circuit shown in Figure 1 for reference.

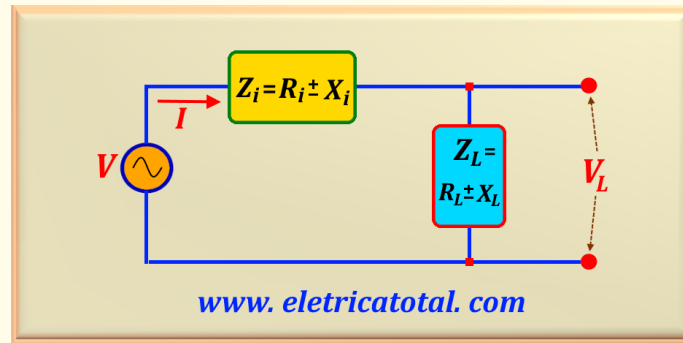


Figura 1: Circuit as reference

So, we can write that:

$$I = \frac{V}{Z_i + Z_L} \quad (3)$$

Now that we know the value of  $I$ , let's apply the following equation to calculate the power:

$$P = |Z_L| I^2 \quad (4)$$

Substituting the value of  $I$  found in equation (3) into (4), we obtain:

$$P = |Z_L| \left( \frac{V}{Z_i + Z_L} \right)^2 \quad (5)$$

We can perform an algebraic manipulation on equation (5) and find:

$$P = \frac{Z_L}{(Z_i + Z_L)^2} V^2 \quad (6)$$

Let's assume, based on the circuit shown in Figure 1, that we have a voltage source and a fixed complex impedance in a series association, supplying power to a load. Let us consider the charge a variable complex impedance. This way, we can have three distinct cases. Let's analyze each case separately.

## Case 1 - We have $R_L \neq 0$ e $X_L = 0$

This is the case where the load is **purely resistive**. So let's go recalculate the value of the electric current by replacing  $Z_L$  with  $R_L$ . Therefore:

$$I = \frac{V}{Z_i + R_L} = \frac{V}{(R_i + R_L) + j X_i} \quad (7)$$

But, to calculate the power, we need to know the absolute value of electrical current. So, we have:

$$|I| = \frac{V}{\sqrt{(R_i + R_L)^2 + X_i^2}} \quad (8)$$

Then the power delivered to the load  $R_L$  will be:

$$P = |Z_L| I^2 = \frac{R_L}{(R_i + R_L)^2 + X_i^2} V^2 \quad (9)$$

As we want to find for which value of  $R_L$  we will obtain the maximum power transfer to the load, we must calculate the first derivative of the above equation in relation to  $R_L$  and equate its result to **zero**. Like this:

$$\frac{dP}{dR_L} = V^2 \left\{ \frac{[(R_i + R_L)^2 + X_i^2] - 2 R_L (R_i + R_L)}{[(R_i + R_L)^2 + X_i^2]^2} \right\} = 0 \quad (10)$$

Obviously, for this expression to be null, we must have the numerator equal to **zero**. Working the numerator algebraically we find the following expression:

$$R_i^2 + 2 R_i R_L + R_L^2 + X_i^2 - 2 R_i R_L - 2 R_L^2 = 0 \quad (11)$$

Performing the necessary algebraic operations to simplify the expression we arrive at:

$$R_i^2 + X_i^2 = R_L^2 \quad (12)$$

This way, we arrive at the final form, that is:

$$R_L = \sqrt{R_i^2 + X_i^2} = |Z_i| \quad (13)$$

Therefore, we conclude that to achieve maximum transfer of power for a purely resistive load, its value must be equal to the absolute value of the impedance of the circuit that connects the load to the voltage source.

## Case 2 - We have $R_L \neq 0$ e $X_L \neq 0$

This is the case where the load has a resistive element **fixed** and reactive **variable**. Then, calculating the value of the electric current we have:

$$I = \frac{V}{Z_i + Z_L} \quad \text{ou} \quad |I| = \frac{V}{\sqrt{(R_i + R_L)^2 + (X_i + X_L)^2}} \quad (14)$$

And the power value is given by:

$$P = R_L |I|^2 \quad (15)$$

Substituting equation (14) into (15), we obtain:

$$P = \frac{R_L}{(R_i + R_L)^2 + (X_i + X_L)^2} V^2 \quad (16)$$

Note that in this case, the value of  $R_L$  is fixed. So, let's derive equation (16) with respect to  $X_L$  and we will consider  $R_L$  constant. Then:

$$\frac{dP}{dX_L} = V^2 \left\{ \frac{-2R_L(X_i + X_L)}{[(R_i + R_L)^2 + (X_i + X_L)^2]^2} \right\} = 0 \quad (17)$$

As  $R_L$  and  $V$  have fixed values, the only way we can cancel this derivative is if:

$$\boxed{X_L = -X_i} \quad (18)$$

In other words, the load value must be the **complex conjugate** of the impedance  $Z_i$ .

### Case 3 - We have $R_L \neq 0$ e $X_L \neq 0$

This is the case where the load has a resistive element **variable** and reactive **fixed**. If we do the calculations for the electric current and power we will find the same values as in case 2. Therefore:

$$P = \frac{R_L}{(R_i + R_L)^2 + (X_i + X_L)^2} V^2 \quad (19)$$

Note that in this case, the value of  $X_L$  is fixed. So, let's derive equation (19) with respect to  $R_L$  and we will consider  $X_L$  constant. Then:

$$\frac{dP}{dX_L} = V^2 \left\{ \frac{(R_i + R_L)^2 + (X_i + X_L)^2 - 2R_L(R_i + R_L)}{[(R_i + R_L)^2 + (X_i + X_L)^2]^2} \right\} = 0$$

Performing algebraic simplification operations on the numerator, we arrive at:

$$R_L^2 = R_i^2 + (X_i + X_L)^2 \quad (20)$$

Now, extracting the square root of  $R_L$  we find the condition what we are looking for, that is:

$$\boxed{R_L = \sqrt{(R_i)^2 + (X_i + X_L)^2} = |Z_i + jX_L|} \quad (21)$$

In this way, we conclude that the maximum transfer of power to the load, when  $R_L$  is equal to the absolute value of the circuit impedance.